

EXPERIMENT NO. 6

TITLE: Study of Class A Amplifier operation


OBJECTIVE: To study the operation of Class A amplifier and determine voltage gain.

APPARATUS:

Sl. No.	Instruments/Apparatus	Instrument Serial No.	Range	Quantity
1	Power Amplifier Trainer Kit	NV6522	-	1
2	2 mm patch cords	-	-	6
3	Oscilloscope	SM430	-	1


SETUP DIAGRAM:

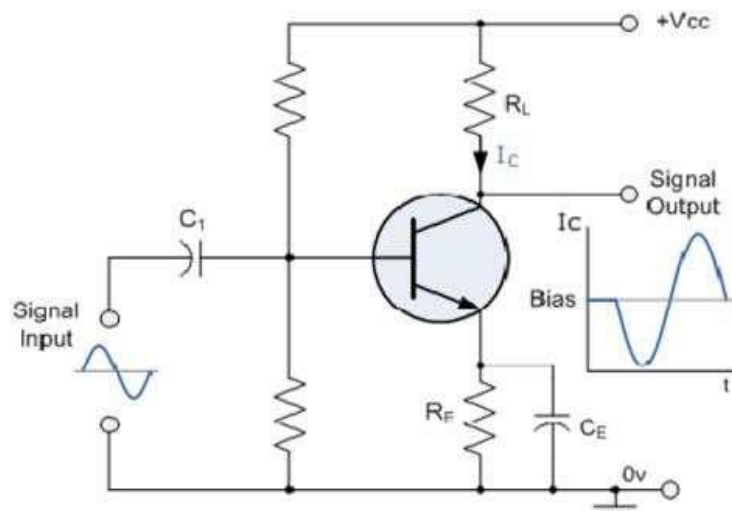Circuit Diagram of class A amplifier is shown below:




OBSERVATIONS:

1) 2V Input Voltage

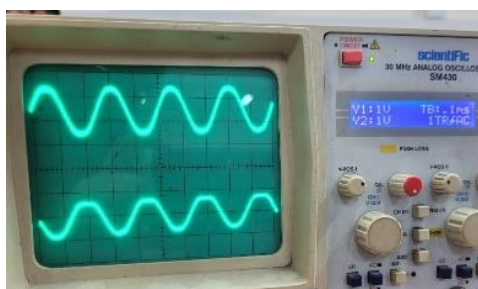


with clipping

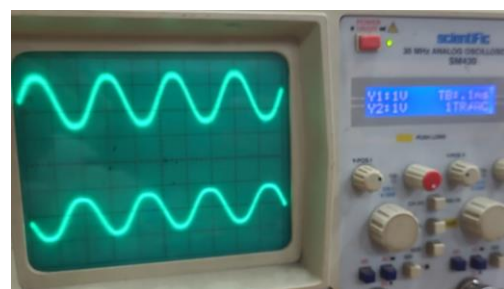


without clipping

2) 2.4V Input Volage

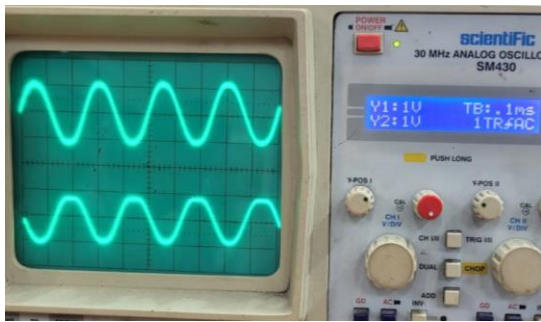


with clipping

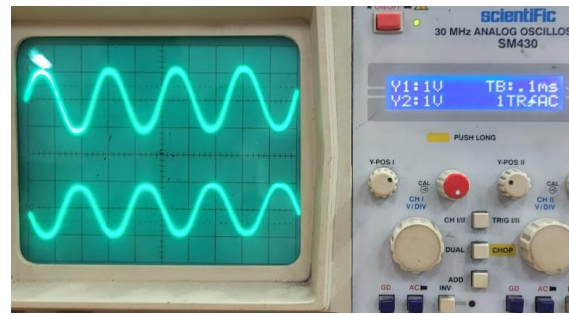


without clipping

3) 3.2V Input Voltage

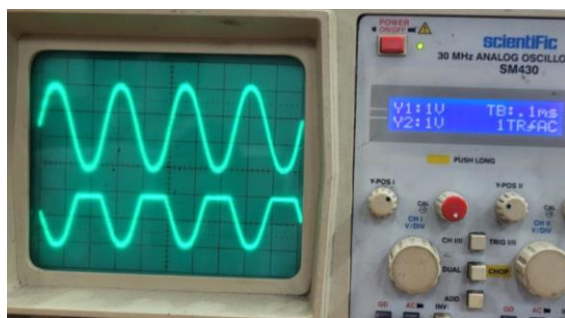


with clipping

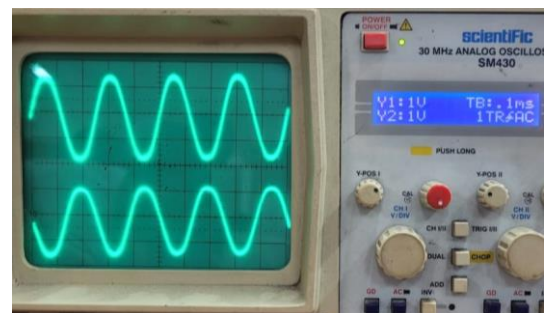


without clipping

4) 4V Input Voltage

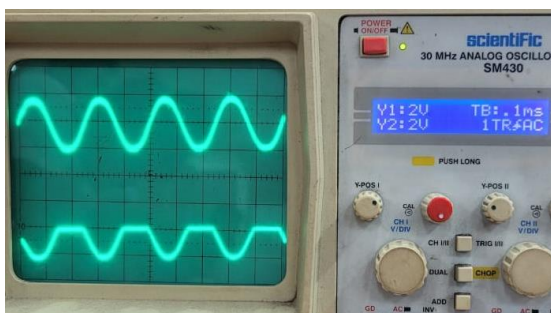


with clipping

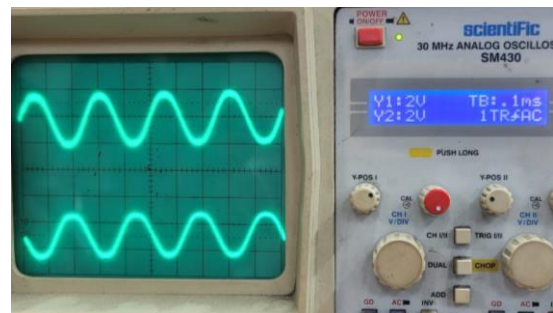


without clipping

5) 8V Input Voltage

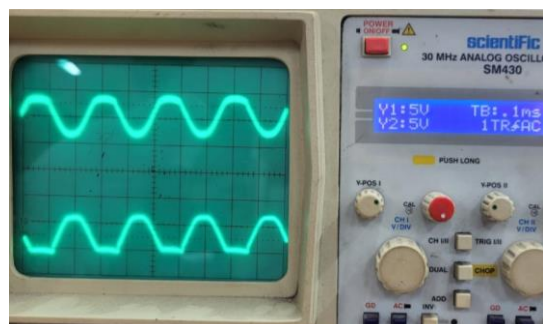

with clipping

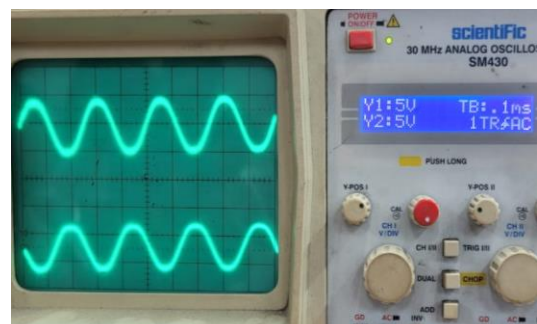

without clipping

DATA SHEET:

23JE0145

Aritra Bera

29/8/24

Expt. 6 - STUDY OF CLASS A AMPLIFIER**Observation Table:**

Sno.	Input Voltage	Output Voltage	Gain
1	2V	1.4V	0.7
2	2.4V	1.8V	0.7
3	3.2V	2V	0.625
4	4V	2.2V	0.55
5	8V	6V	0.75

frequency = 10 KHz

Scale: $V_1 = 1V$ $V_2 = 1V$ **Calculations:**

1) $\frac{V_o}{V_{in}} = \frac{1.4}{2} = 0.7$

2) $\frac{V_o}{V_{in}} = \frac{1.8}{2.4} = 0.7$

3) $\frac{V_o}{V_{in}} = \frac{2}{3.2} = 0.625$

4) $\frac{V_o}{V_{in}} = \frac{2.2}{4} = 0.55$

5) $\frac{V_o}{V_{in}} = \frac{6}{8} = 0.75$

~~XXXXXXXXXX~~
29/8/2024

RESULTS & COMMENTS:

The voltage gain was found to be close to 0.6 or 60% for most input voltages. The output showed very less distortions unlike class B amplifiers, because of its high linearity. This result is consistent with theoretical predictions. The amplifier also had a very simple design consisting of only one BJT transistor. These characteristics make it excellent for applications where the output signal's quality is to be prioritized.