

EXPERIMENT NO. 3


TITLE: Study of op-amp as an Inverting and Non Inverting Summer

OBJECTIVE: To study the Summing operation of Op-amp in inverting and non-inverting configuration.


APPARATUS:

Sl. No.	Instruments/Apparatus	Range	Quantity
1	Experiment Board, ST2322	110-220 V $\pm 10\%$, 50/60 Hz	1
2	Multi meter	1mV-1kV	1
3	Patch Cords	-	3

SETUP DIAGRAM:

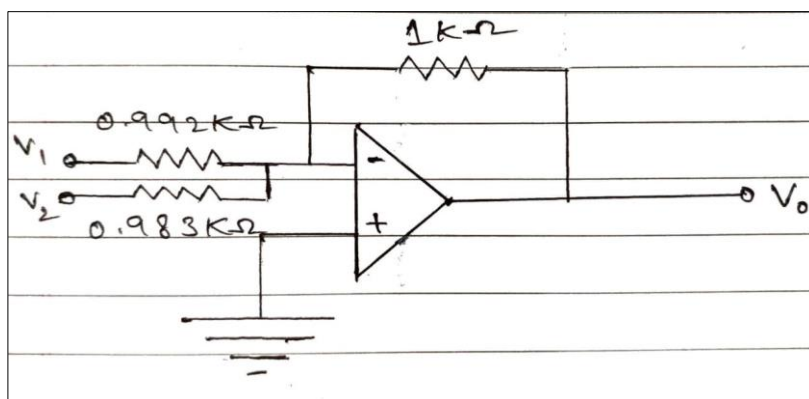

Inverting Summer

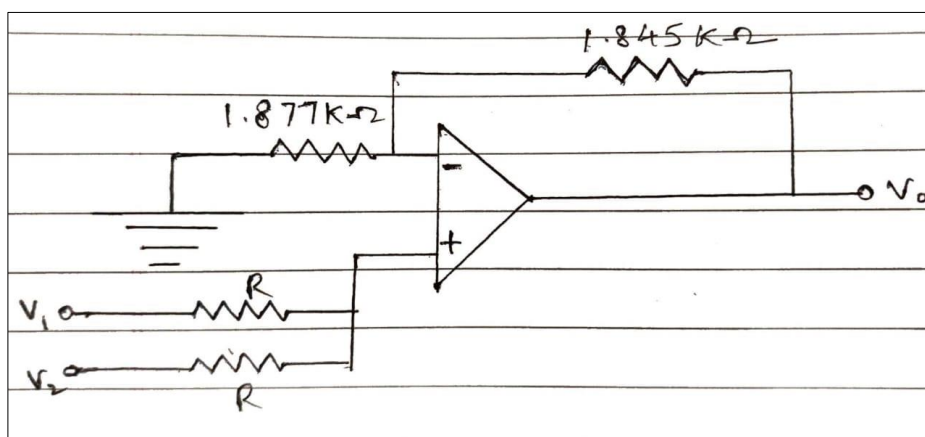

Non-inverting summer

DATA SHEET:

Investing Summes					1/8/24
V_1	V_2	Calculated $V_1 + V_2$	Measured $V_1 + V_2$	Error $\frac{\text{Calculated} - \text{Observed}}{\text{Calculated}} \times 100\%$	
1.105	1.185	-2.319	-2.335	0.67%	
1.45	1.65	-3.14	-3.186	1.4%	
2.126	1.941	-4.117	-4.250	3.23%	
2.55	2.80	-5.42	-5.585	3.04%	
3.005	3.070	-6.152	-6.37	3.54%	
Non-Investing Summes					
V_1	V_2	Calculated $V_1 + V_2$	Measured $V_1 + V_2$	Error $\frac{\text{Calculated} - \text{Obs}}{\text{Calculated}} \times 100\%$	
1.136	2.21	3.318	3.393	2.26%	
1.545	2.86	4.367	4.568	4.6%	
3.00	3.3	6.276	6.58	4.84%	
3.55	3.7	7.19	7.46	3.76%	
4.21	4.032	8.172	8.52	4.26%	
Calculation:					
$V_0 = \left(\frac{V_1 + V_2}{2} \right) \left(1 + \frac{R_f}{R} \right) = \left(\frac{1.136 + 2.21}{2} \right) \left(1 + \frac{1.845}{1.877} \right)$					
= 3.318 V					
from 1/8/24					

RESULTS & COMMENTS:

Op-amp as an inverting and non-inverting summer has been studied and verified.

1. Inverting Summer Configuration: The value of V_o is given by:

$$V_o = -R_f(V_1/R_1 + V_2/R_2)$$

where R_f is the feedback resistor, and R_1 and R_2 are the input resistors.

The calculated values of V_o closely match the measured values, as shown in the data sheet.

2. Non-inverting Summer Configuration: The value of V_o is given by:

$$V_o = [(V_1 + V_2)/2] (1 + R_f/R)$$

where R_f is the feedback resistor, and R is the resistance of the two input resistors.

The calculated values of V_o closely match the measured values, as shown in the data sheet.

Overall, both circuits demonstrated their theoretical principles effectively, with results aligning closely with predictions.