

EXPERIMENT NO. 5

TITLE: Study of Class B Amplifier operation


OBJECTIVE: To study the operation of Class B amplifier and determine crossover distortion span (per cycle) at different loading condition.

APPARATUS:

Sl. No.	Instruments/Apparatus	Instrument Serial No.	Range	Quantity
1	Power Amplifier Trainer Kit	NV6522	-	1
2	2 mm patch cords	-	-	6
3	Oscilloscope	SM430	-	1

SETUP DIAGRAM:

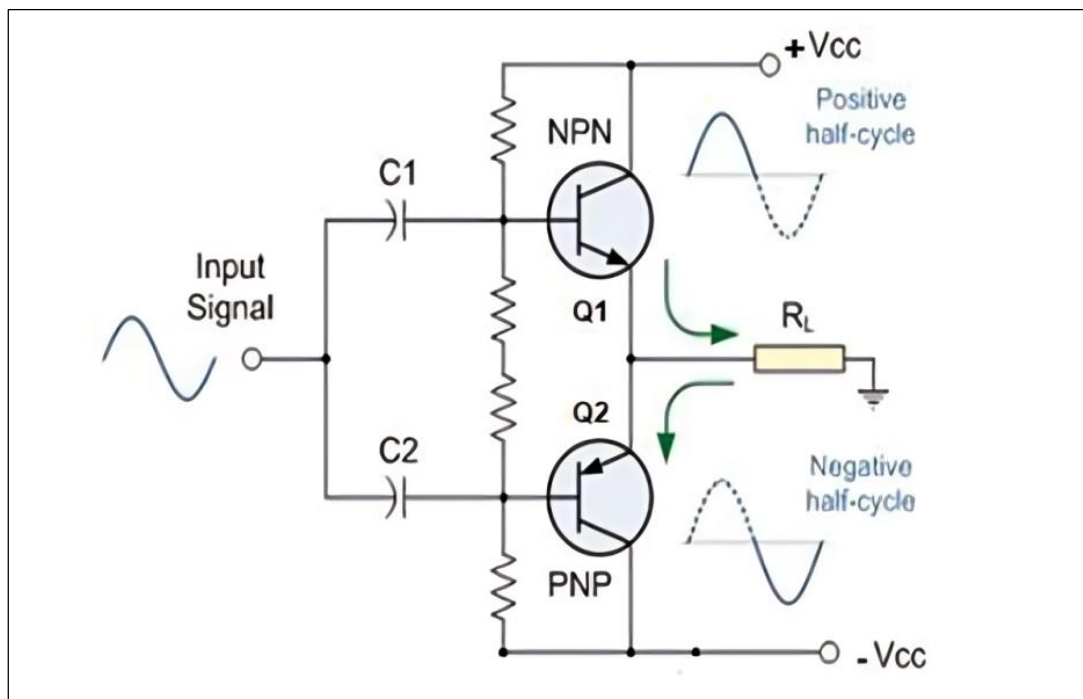Circuit Diagram of class B amplifier is shown below:




DATA SHEET:


Asitara Bera 23JE0145		Exp - 5		STUDY OF CLASS-B AMPLIFIER	
Sl. no.	Frequency	Crossover distortion span (per cycle) in degree	peak magnitude		
			Input Voltage	Output Voltage	
1	10 KHz	144°	2 V _{pp}	1.4 V _{pp}	
2	15 KHz	205.71°	2 V _{pp}	1.3 V _{pp}	
$f = 10 \text{ KHz}$ $360^\circ \rightarrow 10 \text{ div.}$ $\Rightarrow 1 \text{ div} \rightarrow 36^\circ$ Crossover distortion = 4 div $= 4 \times 36 = \underline{144^\circ}$					
$f = 15 \text{ KHz}$ $360^\circ \rightarrow 7 \text{ div.}$ $\Rightarrow 1 \text{ div} \rightarrow (360/7)^\circ$ Crossover distortion = 4 div $= 4 \times \frac{360}{7} = \underline{205.71^\circ}$					

OBSERVATIONS:

1) At $f = 10 \text{ kHz}$

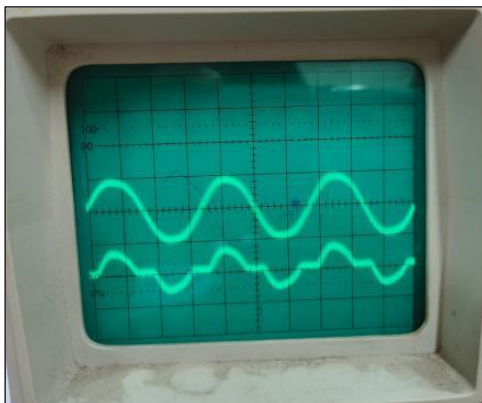

2) At $f = 15 \text{ kHz}$

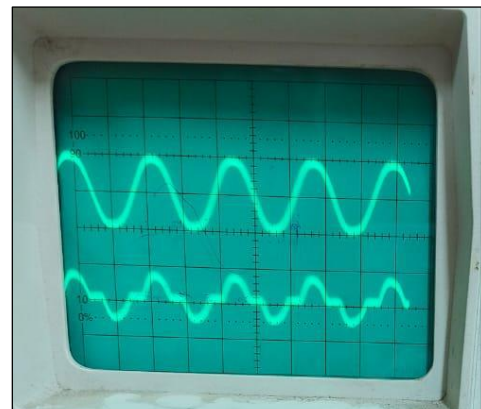

RESULTS & COMMENTS:

In the experiment on Class B amplifiers, we observed that the amplifier achieved a good efficiency ($> 50\%$), consistent with theoretical predictions. The output signal had crossover distortions, which is typical for Class B designs. These findings highlight the Class B amplifier's effective power efficiency and its inherent trade-offs in signal quality, emphasizing the importance of optimizing biasing to reduce distortion.